

# Operational Amplifiers and Applications




# Review

## Fundamentals of basic circuits and what we learned in Chapter 1

The current  $i$  through resistance  $R$  is related to its voltage  $v$  by Ohm's law


$$v = iR$$

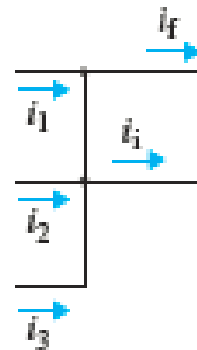According to Kirchhoff's current law, the sum of all currents at a node must be zero, or the currents coming in to the node must equal to the current going out



$$i_1 + i_2 + i_3 = i_f + i_i$$

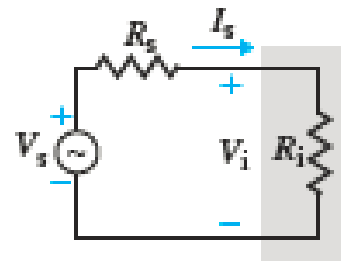
According to the voltage divider rule between two resistances  $R_s$  and  $R_i$ , the output voltage  $V_i$  across resistance  $R_i$  is related to the input voltage  $V_s$  by



$$V_i = \frac{R_i}{R_i + R_s} V_s$$
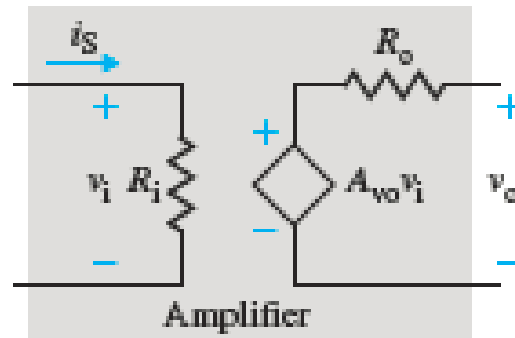
# Review

The model and parameters of a voltage amplifier are




Voltage gain  $A_{vo}$ ,  
Input resistance  $R_i$ ,  
output resistance  $R_o$

If voltage amplifiers with gains of  $A_1, A_2, \dots, A_n$  are cascaded, the overall gain is the product of the gain of each stage.

$$A_{vo} = A_1 A_2 \dots A_n$$

# Review

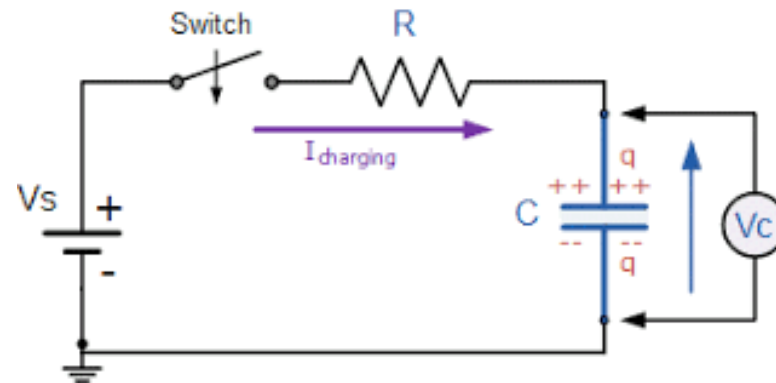

The instantaneous current  $i(t)$  through an RC circuit for a step voltage  $V_s$

$$i = \frac{V_s}{R}(1 - e^{-t/RC})$$

The voltage  $v_c$  of a capacitor  $C$  is related to its current  $i$  by

$$v_c = \frac{1}{C} \int i \, dt$$

The current  $i$  of a capacitor  $C$  is related to its voltage  $v_c$  by

$$i = C \frac{dv_c}{dt}$$



# Review

The impedance of a capacitor at a frequency $\omega$ or $f$ , $X_C$	$X_C = \frac{1}{j\omega C} \text{ or } \frac{1}{j2\pi fC}$
The cutoff frequency of an RC circuit	$f_L = \frac{1}{2\pi RC}$
The cutoff frequency is defined as the frequency at which the gain rises or falls to 70.7% ( $1/\sqrt{2}$ ) of the band-pass gain, $A_{BP}$ .	70.7% ( $1/\sqrt{2}$ )
The vector representation of a sinusoidal voltage with a peak magnitude $V_m$ , $V_m \sin(2\pi ft + \varphi)$	$V_m \angle \varphi$
The derivative of $V_m \sin(\omega t)$ , $\frac{d}{dt} (V_m \sin \omega t)$	$\omega V_m (\cos \omega t)$ , or $\omega V_m \angle 90^\circ$


# Characteristics of Ideal Op-Amps - Op-Amp Circuit Model

- The output voltage of an op-amp is directly proportional to the small-signal differential input voltage.

$$v_o = A_o v_d = A_o (v_p - v_n)$$

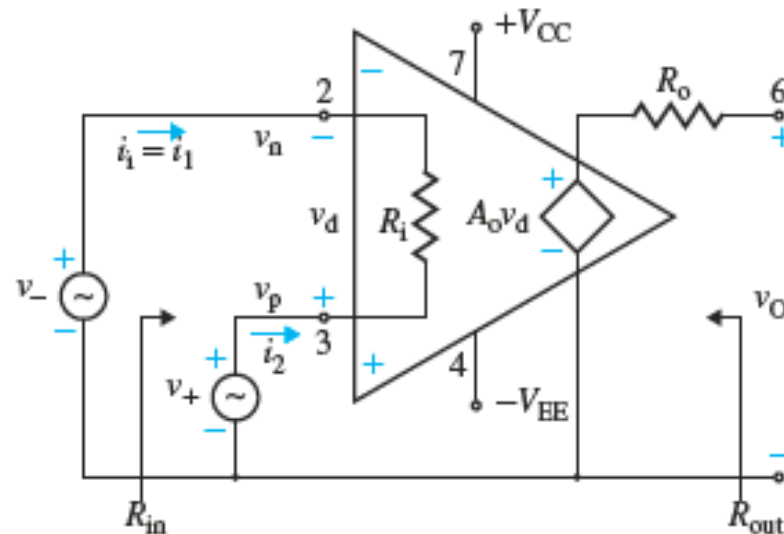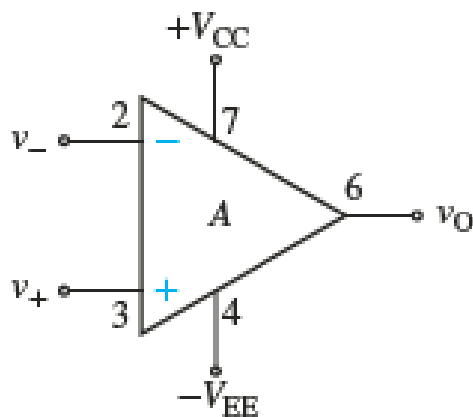


(a) Equivalent circuit

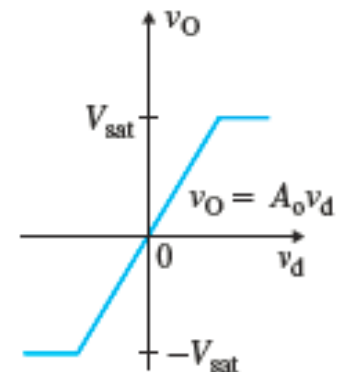

(b) Transfer characteristic
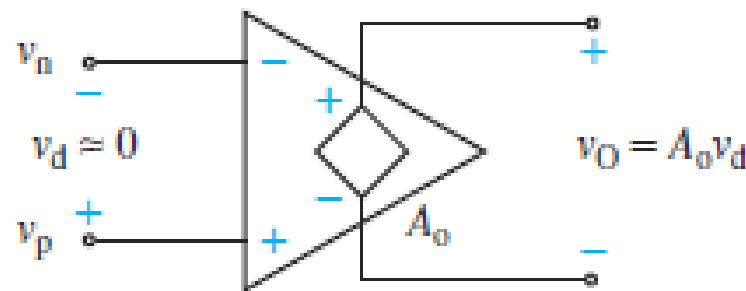
# Ideal Op-Amp Model


- The open-loop voltage gain is infinite:  $A_o = \infty$ .
- The input resistance is infinite:  $R_i = \infty$ .
- The amplifier draws no current:  $i_i = 0$ .
- The output resistance is negligible:  $R_o = 0$ .
- The gain  $A_o$  remains constant and is not a function of frequency.
- The output voltage does not change with changes in power supplies. This condition is generally specified in terms of the power supply sensitivity (PSS):  $PSS = 0$ .


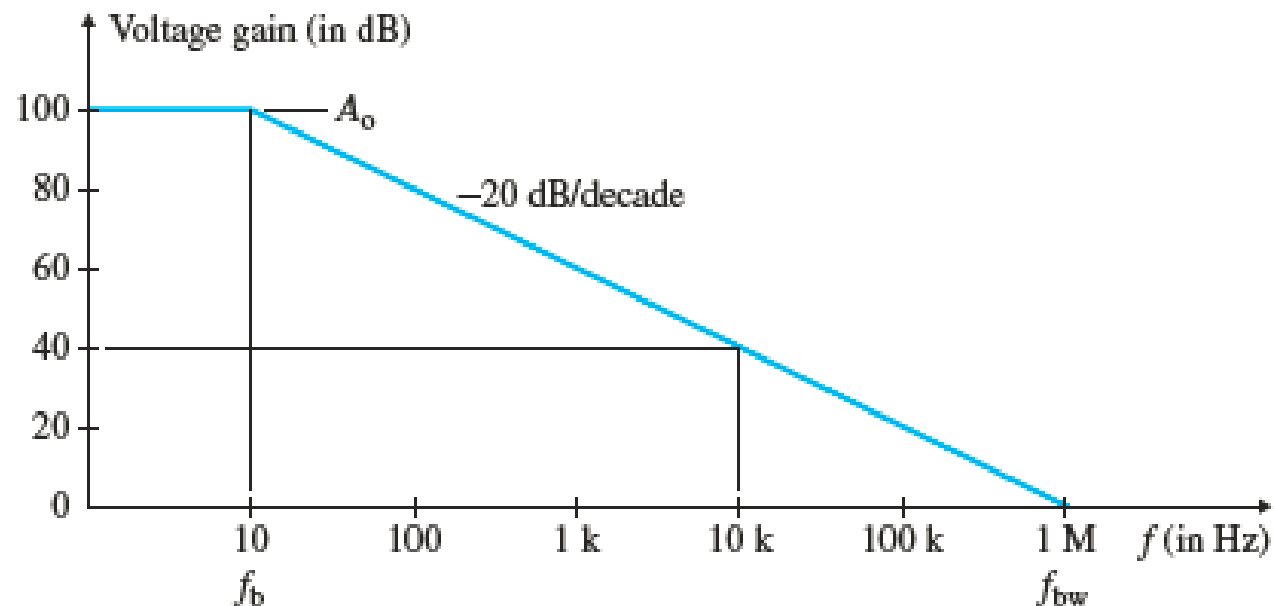
# Op-Amp Frequency Response

- The differential voltage gain of an op-amp has the highest value at DC or low frequencies. The gain decreases with frequency.

$$A_o(j\omega) = \frac{A_o}{1 + j\omega / \omega_b} = \frac{A_o}{1 + jf / f_b}$$






# Non-inverting Amplifiers


- The input voltage is connected directly to the noninverting terminal.
- Closed-loop voltage gain  $A_f$ :

$$A_f = \frac{v_o}{v_s} = 1 + \frac{R_F}{R_1}$$
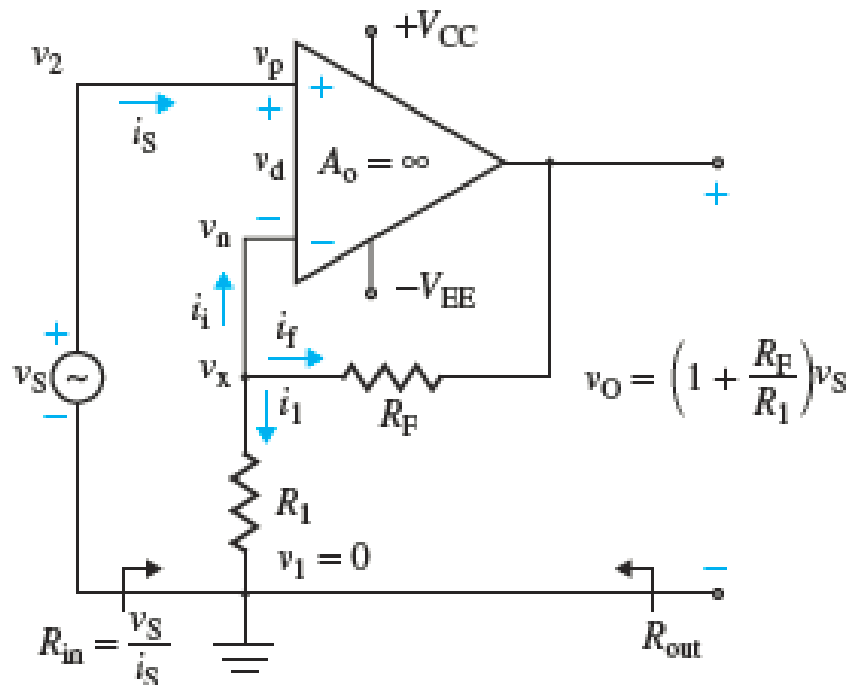
$$v_x = \frac{R_1}{R_1 + R_F} v_o = v_s$$



(a) Noninverting configuration

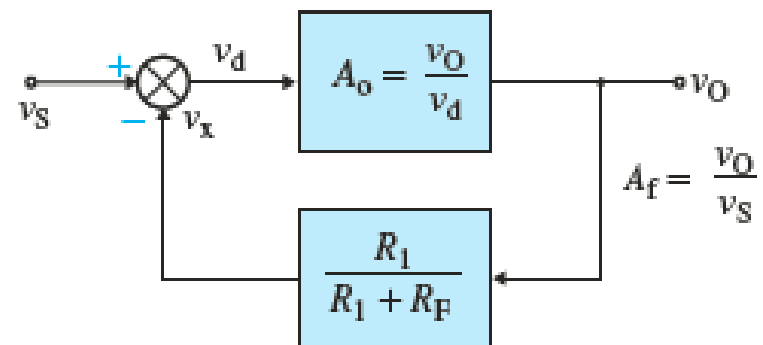

(b) Closed-loop feedback

# Input and Output Resistances

- Since the current drawn by the amplifier is zero, the effective input resistance of the amplifier is very high, tending to infinity.


$$R_{in} = \frac{v_S}{i_S} = \infty$$

- The effective output resistance:

$$R_{out} = R_o \approx 0$$
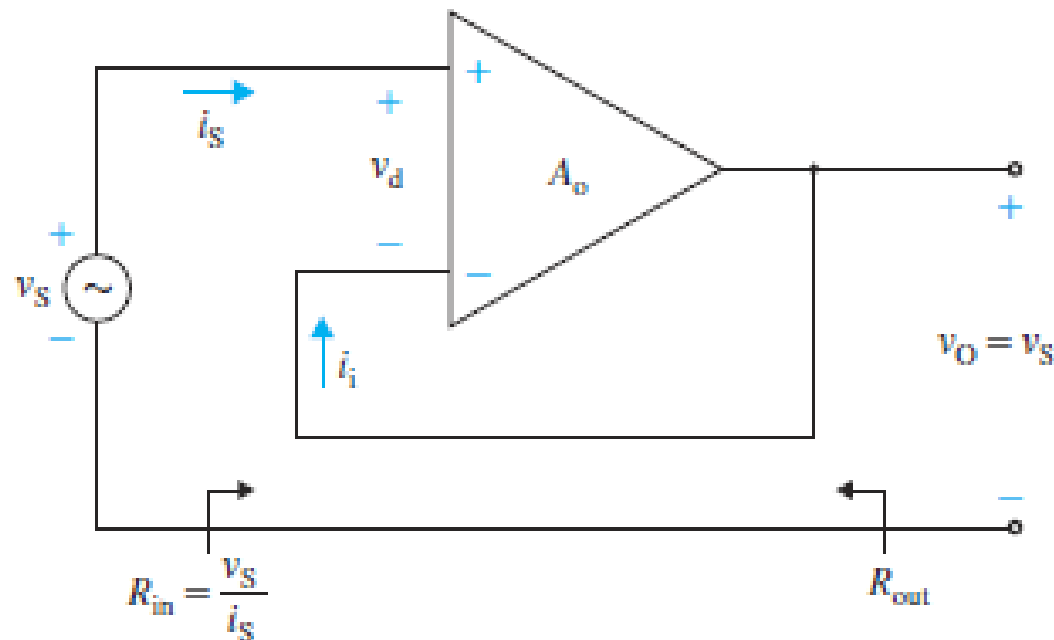
# Voltage Follower

- If  $R_F = 0$  or  $R_1 = \infty$  then  $A_f = 1$
- Used as the *buffer stage* between a low impedance load and a source requiring a high impedance load.




# Non-inverting Summing Amplifiers

$$v_p = \frac{R_b \parallel R_c}{R_a + R_b \parallel R_c} v_a + \frac{R_a \parallel R_c}{R_b + R_a \parallel R_c} v_b + \frac{R_a \parallel R_b}{R_c + R_a \parallel R_b} v_c$$

$$v_o = \left(1 + \frac{R_F}{R_B}\right) \left(\frac{R_A}{R_a} v_a + \frac{R_A}{R_b} v_b + \frac{R_A}{R_c} v_c\right)$$

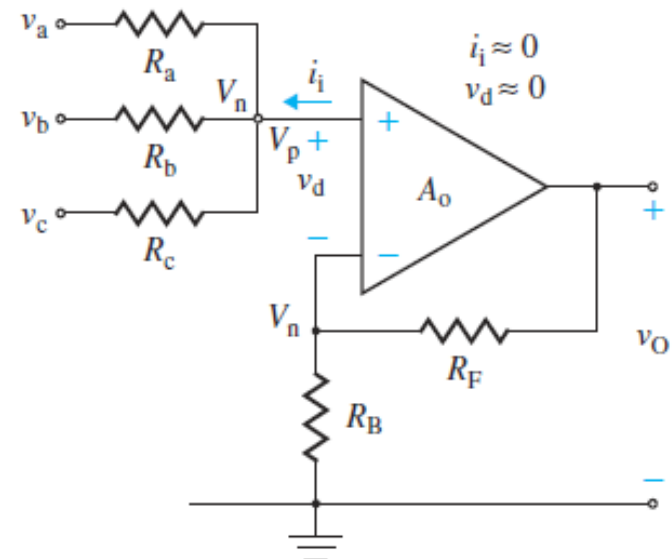where  $R_A = (R_a \parallel R_b \parallel R_c)$




# Inverting Amplifiers

- The input voltage is connected to the inverting terminal and the non-inverting terminal is connected to the ground directly or through a resistance.

- Closed-Loop Gain:  $A_f = \frac{v_O}{v_S} = -\frac{R_F}{R_1}$

$$\frac{v_O}{R_F} = -\frac{v_S}{R_1}$$

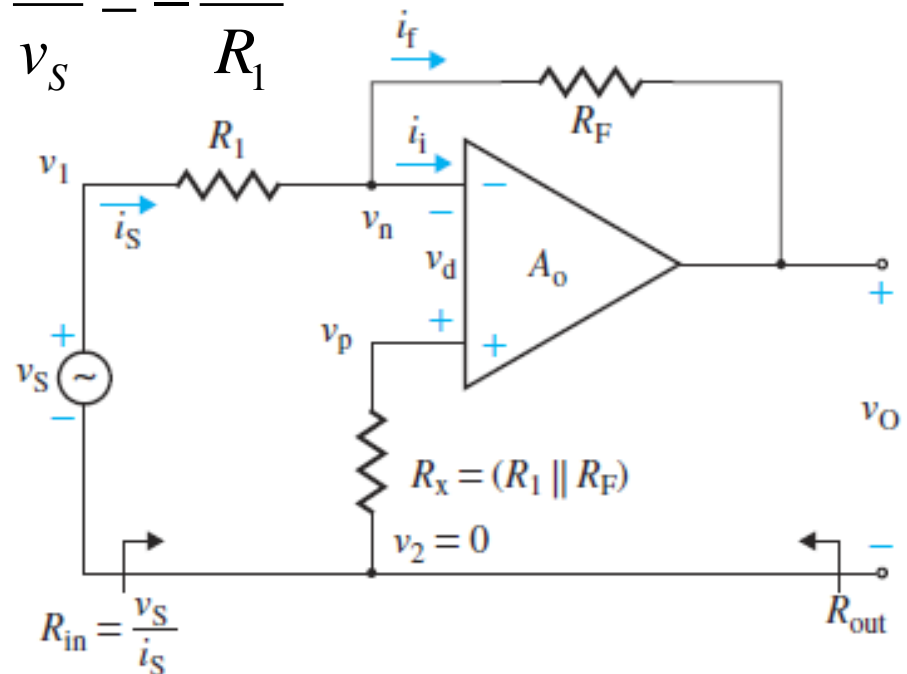


# Input and Output Resistances

- The effective input resistance  $R_{in}$  of the amplifier:

$$R_{in} = \frac{v_S}{i_S} = \frac{v_S}{(v_S + v_d) / R_1} \approx R_1$$

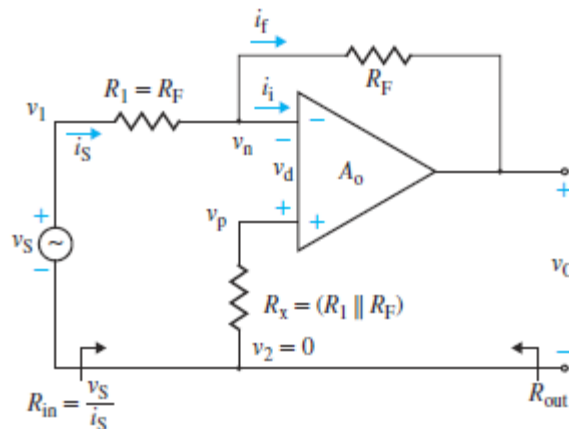- Op-Amp Inverter:** An inverter is often used to invert the polarity of a signal.



# Effect of Finite Op-Amp Gain on Closed-Loop Gain


- Closed-loop voltage gain:

$$A_f = \frac{v_O}{v_S} = -\frac{R_F / R_1}{1 + (1 + R_F / R_1) / A_o} = -\frac{R_F}{R_1(1 + x)}$$
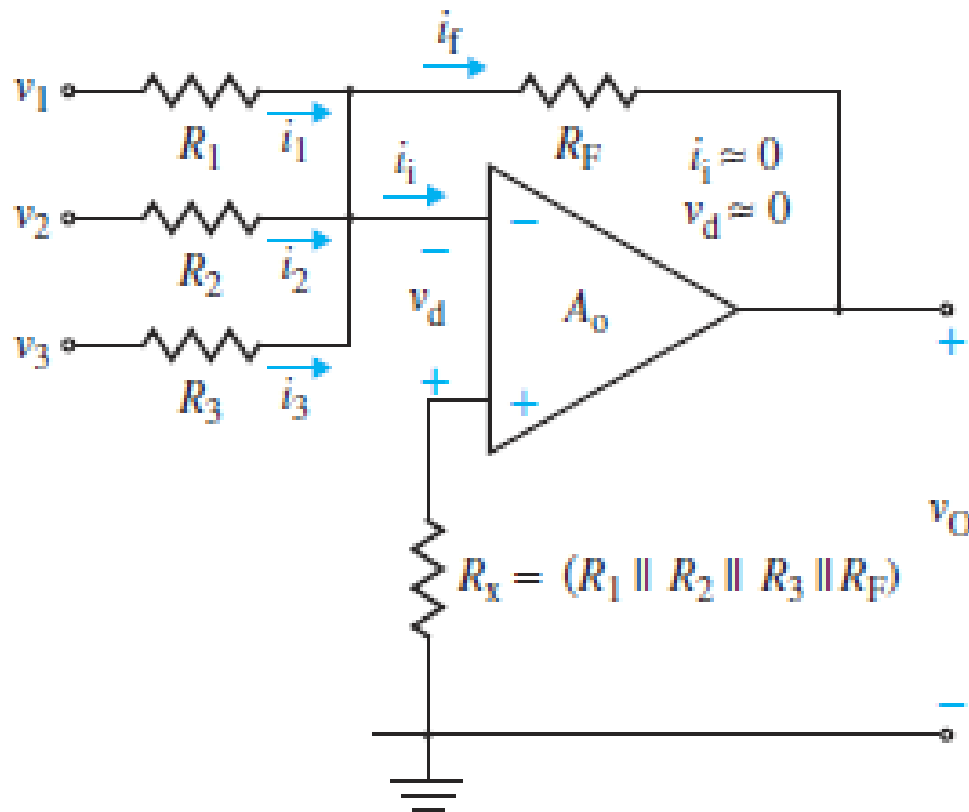
# Inverting Summing Amplifiers

- Output voltage:

$$v_o = -\left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3\right)$$





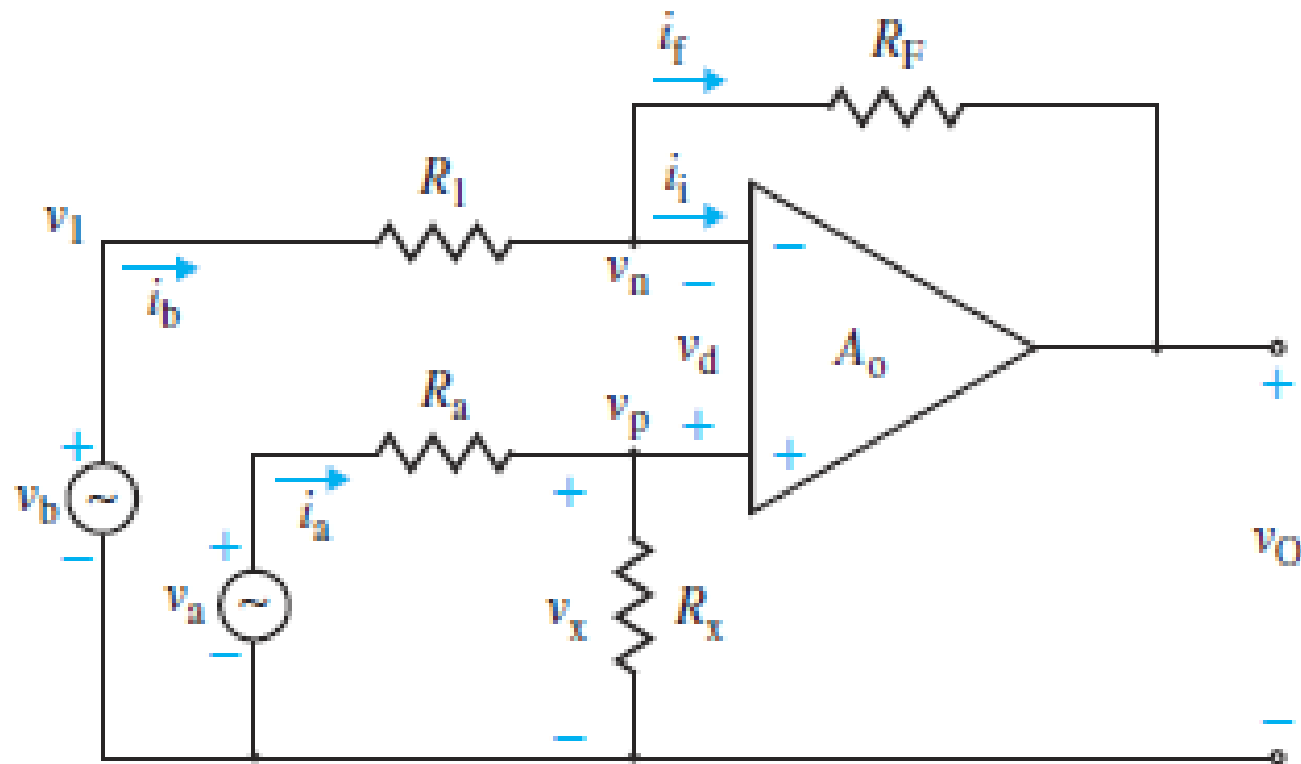
# Difference Amplifiers


- Two input voltages ( $v_a$  and  $v_b$ ) are applied—one to the non-inverting terminal and another to the inverting terminal.
- Closed-Loop Gain of Difference Amplifiers:

$$v_o = -\frac{R_F}{R_1} v_b + \left(1 + \frac{R_F}{R_1}\right) \left(\frac{R_x}{R_x + R_a}\right) v_a$$


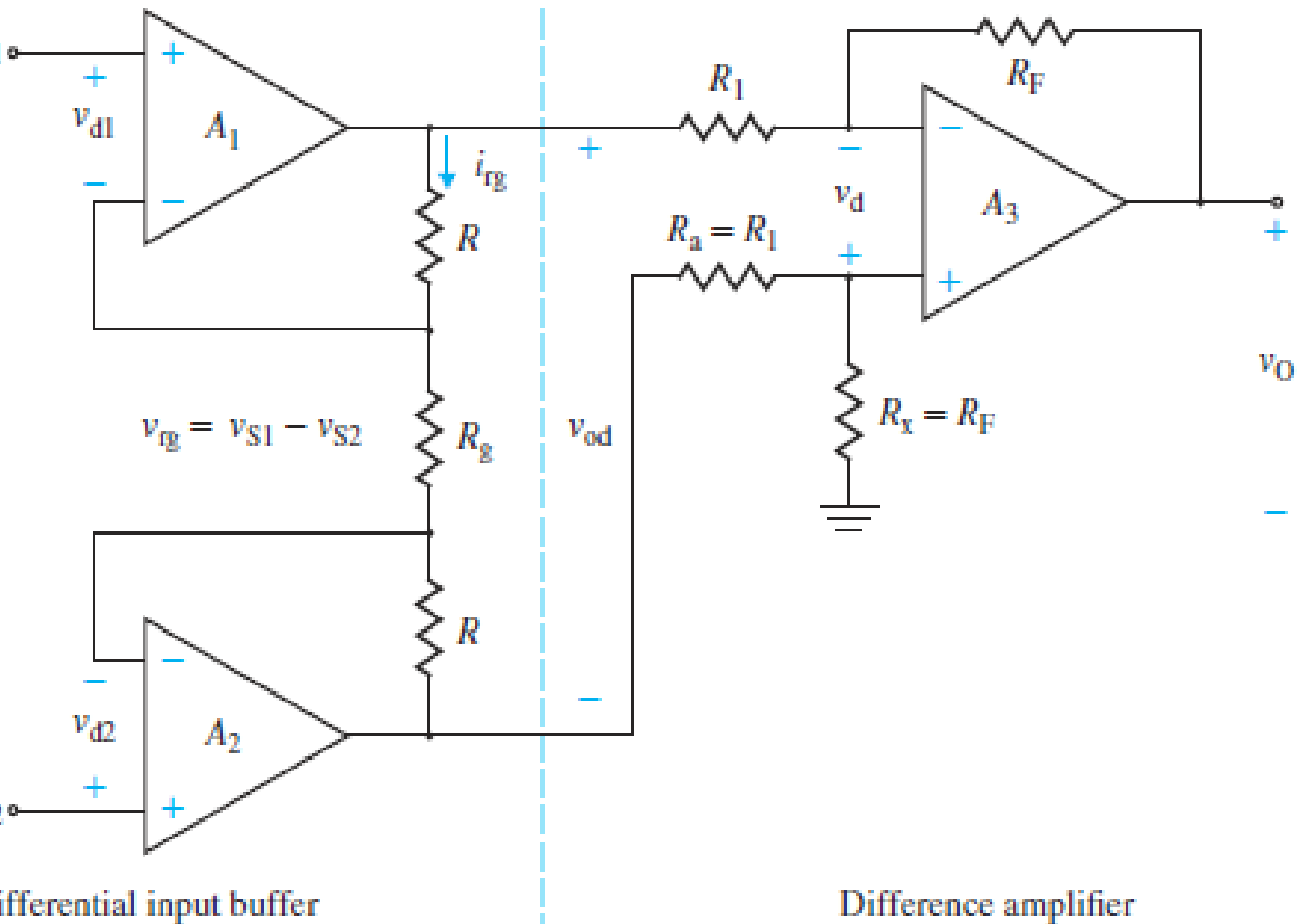
# Instrumentation Amplifiers

- **Instrumentation amplifier:** dedicated difference amplifier with an extremely high input impedance.
- Its gain can be precisely set by a single resistance.
- Closed-Loop Gain of Instrumentation Amplifiers:



# Instrumentation Amplifiers

$$v_{od} = i_{rg}(R_g + 2R) = \frac{v_{S1} - v_{S2}}{R_g}(R_g + 2R) = (v_{S1} - v_{S2})\left(1 + \frac{2R}{R_g}\right)$$

Using Eq. (3.82), we can calculate the output voltage  $v_O$  as


$$v_O = -v_{od}\frac{R_F}{R_1} = -(v_{S1} - v_{S2})\left(1 + \frac{2R}{R_g}\right)\left(\frac{R_F}{R_1}\right)$$

$$A_f = \left(1 + \frac{2R}{R_g}\right)\left(\frac{R_F}{R_1}\right)$$

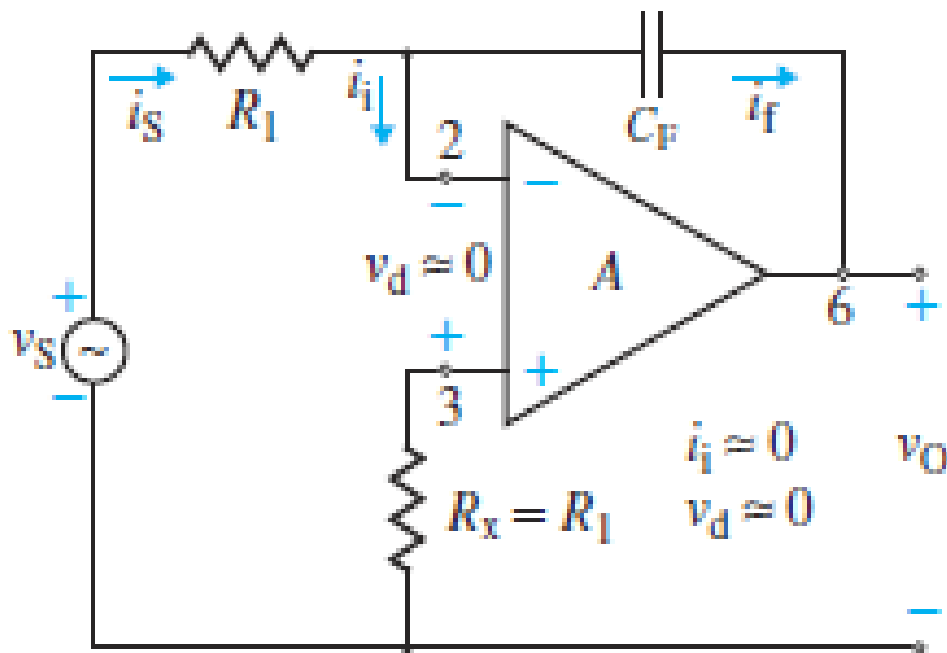
# Integrators

- If the resistance  $R_F$  in the inverting amplifier is replaced by a capacitance  $C_F$ , the circuit will operate as an integrator.

$$v_O(t) = -\frac{1}{R_1 C_F} \int_0^t v_S dt - v_C(t=0)$$




(a) Circuit

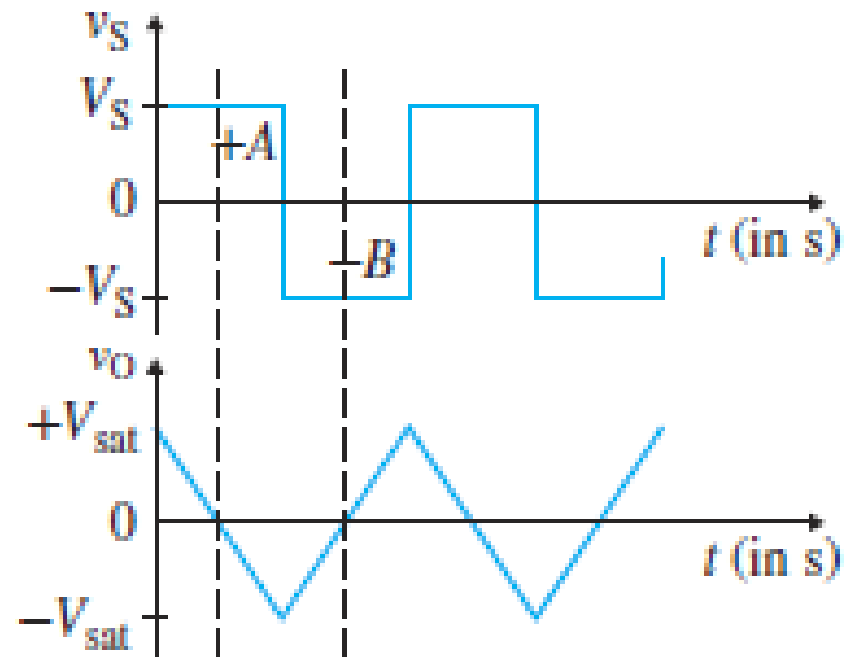

(b) Waveforms
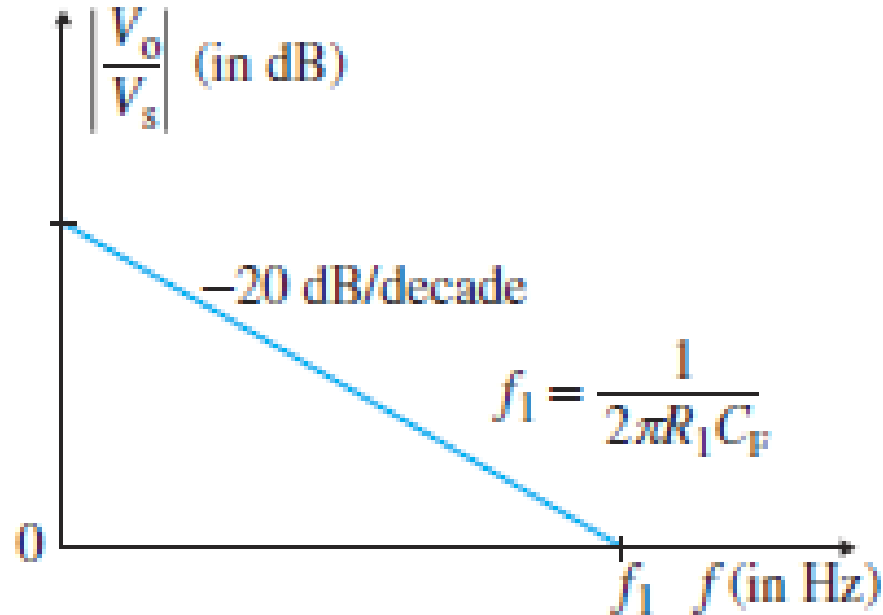
# Integrators

$$v_o(t) = -\frac{1}{R_1 C_F} \int_0^t v_s dt - v_C(t=0)$$




(c) Magnitude plot
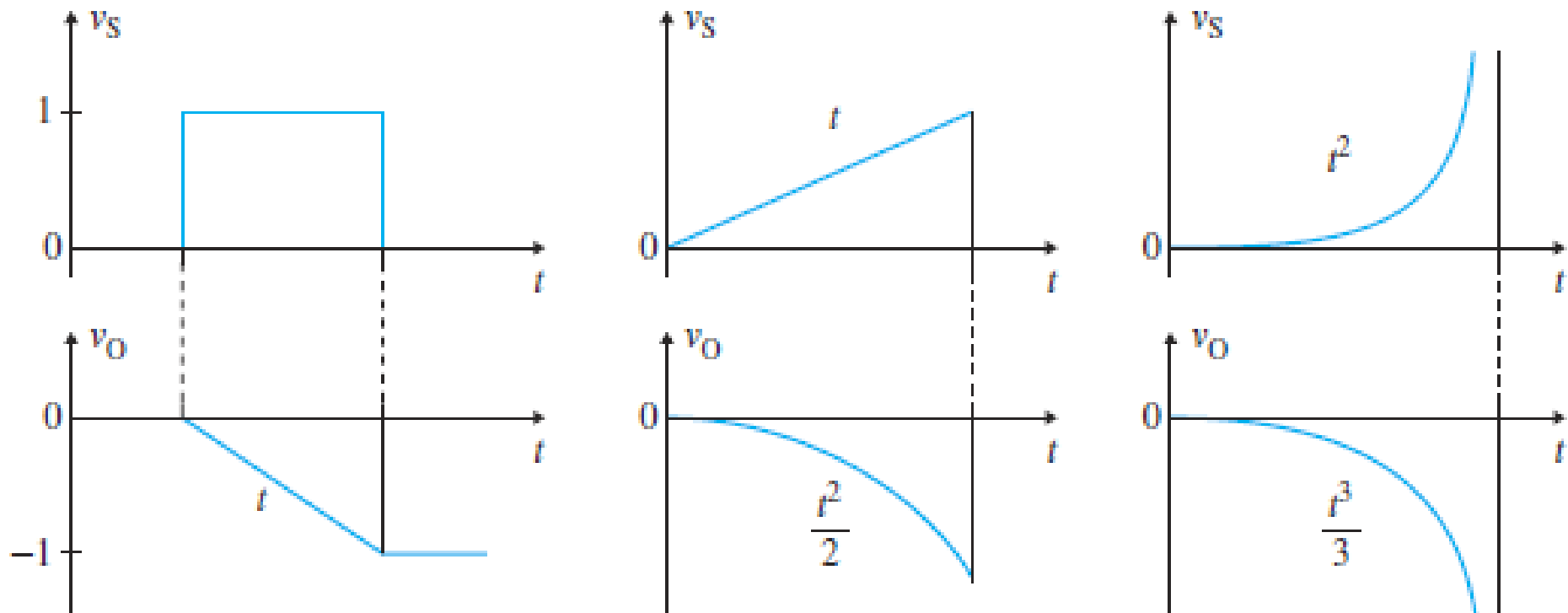
# Frequency Response of an Ideal Integrator

- The voltage gain:

$$A_f(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = -\frac{1}{j\omega C_F R_1}$$




# Closed-Loop Gain of a Practical Integrator

- **Voltage gain:**


$$A_f(j\omega) = \frac{V_o(j\omega)}{V_s(j\omega)} = -\frac{R_F / R_1}{1 + j\omega C_F R_F}$$

- **The cutoff frequency:**

$$f_H = -\frac{1}{2\pi R_F C_F}$$

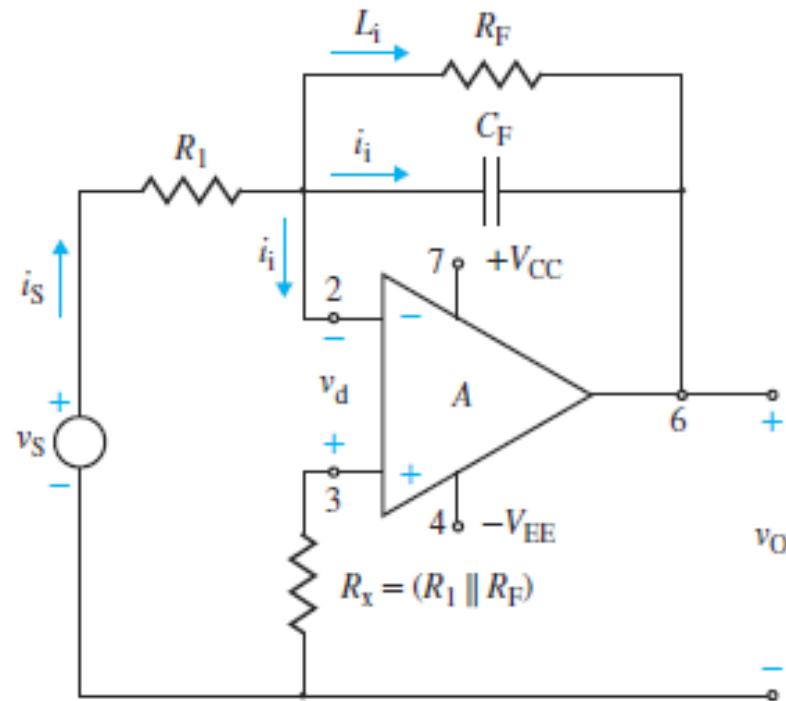

(a) Circuit

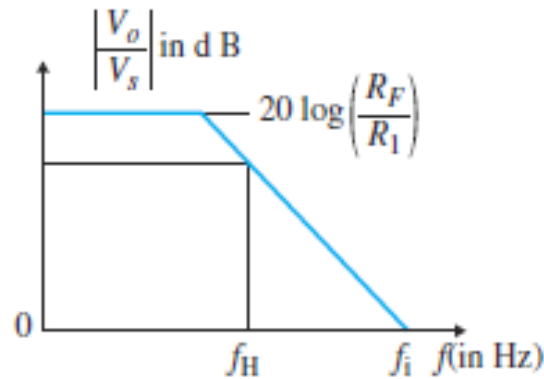


(b) Magnitude plot

y


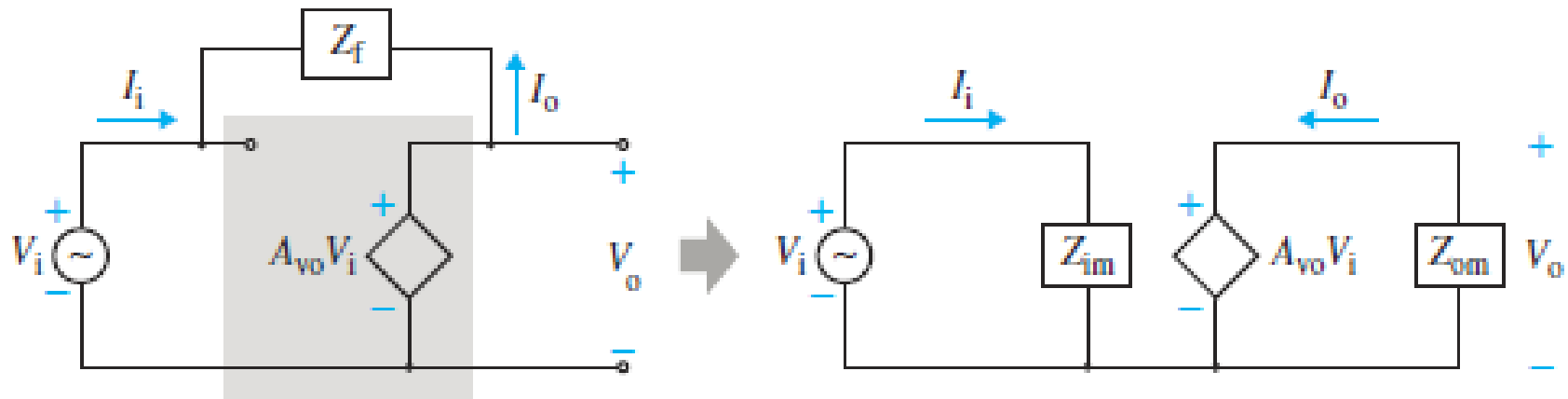
# Miller's Theorem and Capacitance

- Miller's theorem simplifies the analysis of feedback amplifiers.
- If an impedance is connected between the input side and the output side of a voltage amplifier, this impedance can be replaced by two equivalent impedances—one connected across the input and the other connected across the output terminals.



(a) Feedback amplifier

(b) Miller equivalent

# Miller's Theorem and Capacitance (cont'd)

- Output impedance  $Z_{om}$  :

$$Z_{om} = \frac{V_o}{I_o} = \frac{Z_f}{1 - 1/A_{vo}}$$

- Equivalent Miller's input and output capacitances:


$$C_{im} = (1 - A_{vo})C_F$$

$$C_{om} = (1 - 1/A_{vo})C_F$$


# Differentiators

- If the resistance  $R_1$  in the inverting amplifier is replaced by a capacitance  $C_1$
- Closed-Loop Gain of an Ideal Differentiator:

$$v_O = -R_F C_1 \frac{dv_S}{dt}$$

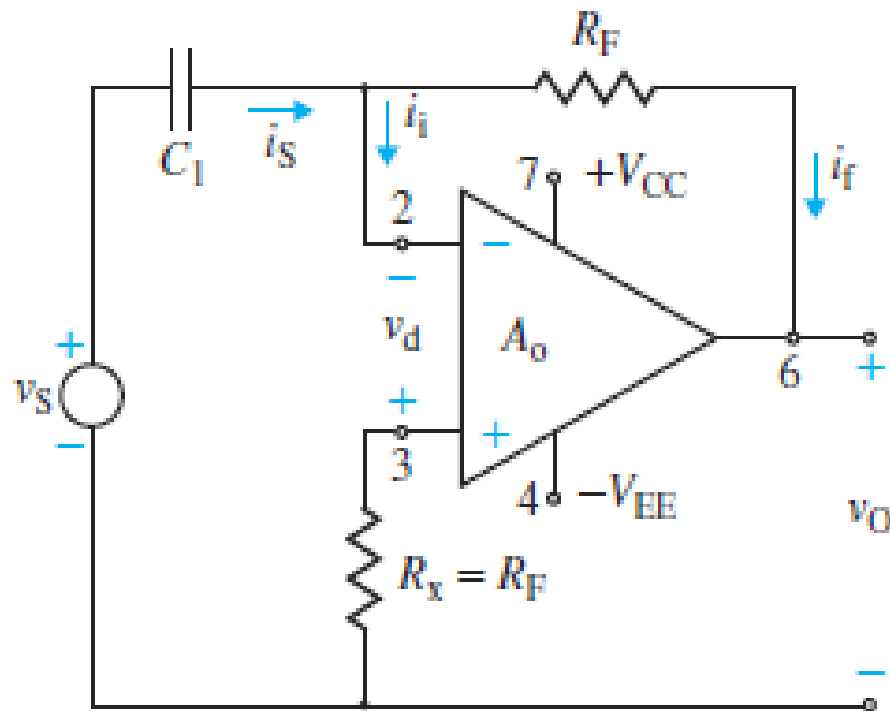

(a) Circuit

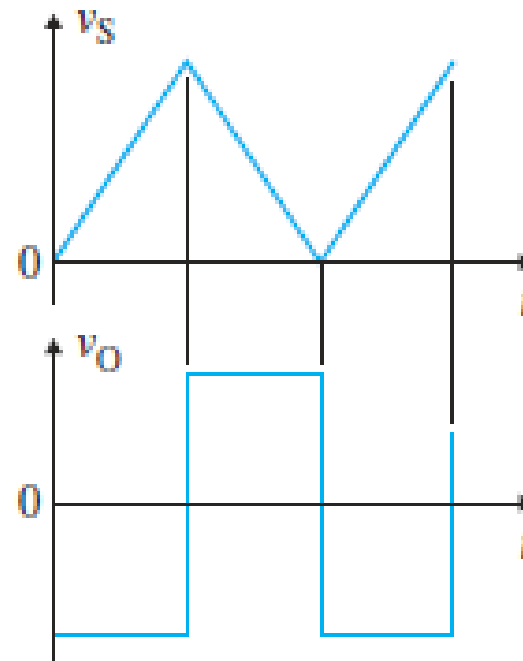


(b) Waveforms

# Differentiators

- If the resistance  $R_1$  in the inverting amplifier is replaced by a capacitance  $C_1$
- Closed-Loop Gain of an Ideal Differentiator:

$$v_O = -R_F C_1 \frac{dv_S}{dt}$$

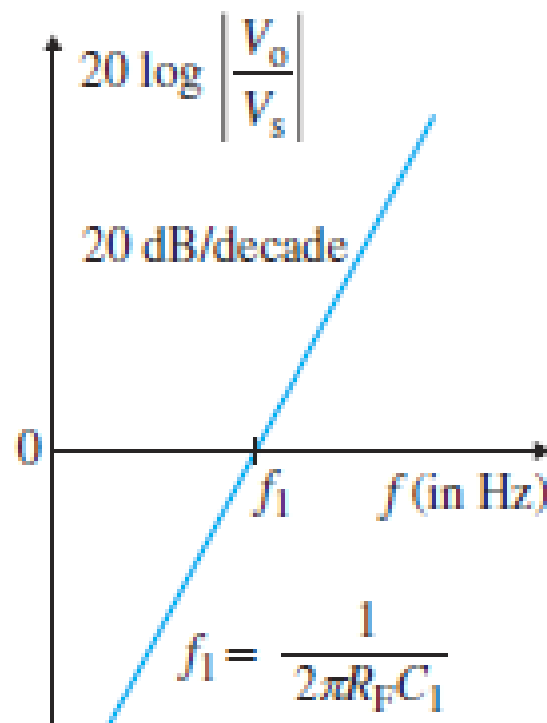


(c) Magnitude plot

or duplicated, or posted to a publicly

# Frequency Response of an Ideal Differentiator


$$A_f(j\omega) = -j\omega C_1 R_F$$

- Voltage gain:

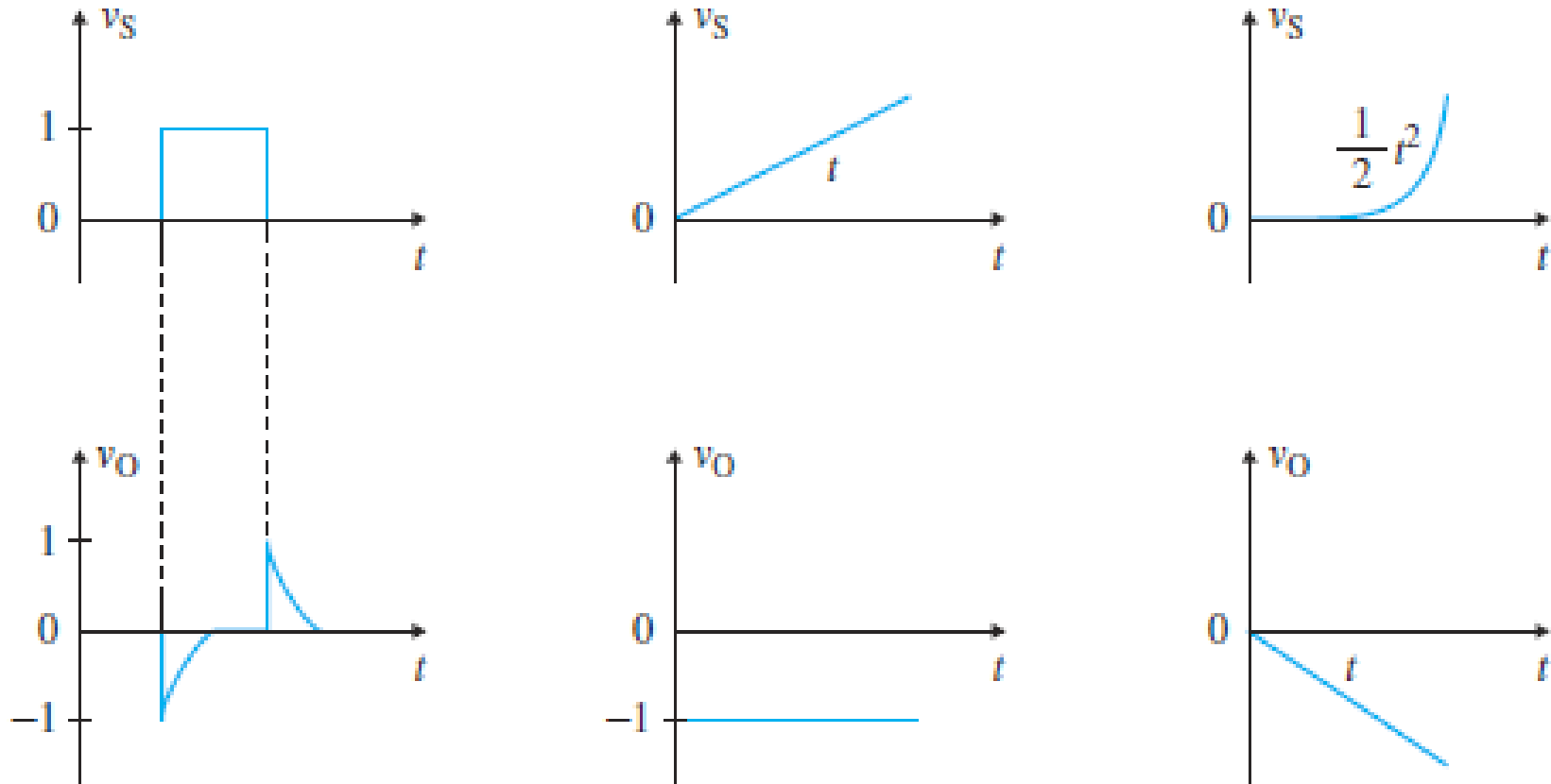

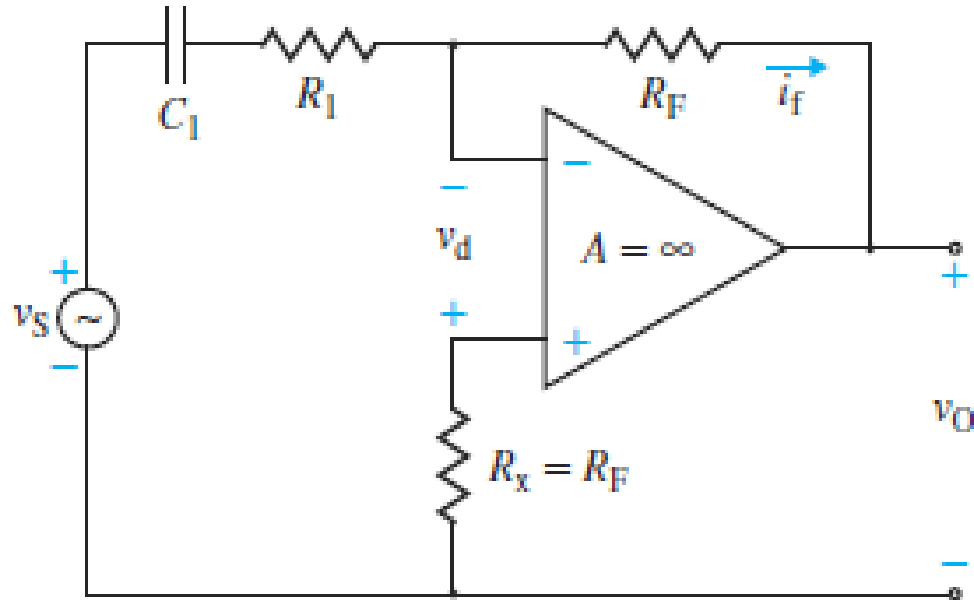
# Closed-Loop Gain of a Practical Differentiator

$$A_f(j\omega) = -\frac{R_F C_1 j\omega}{1 + j\omega R_1 C_1}$$



(a) Circuit

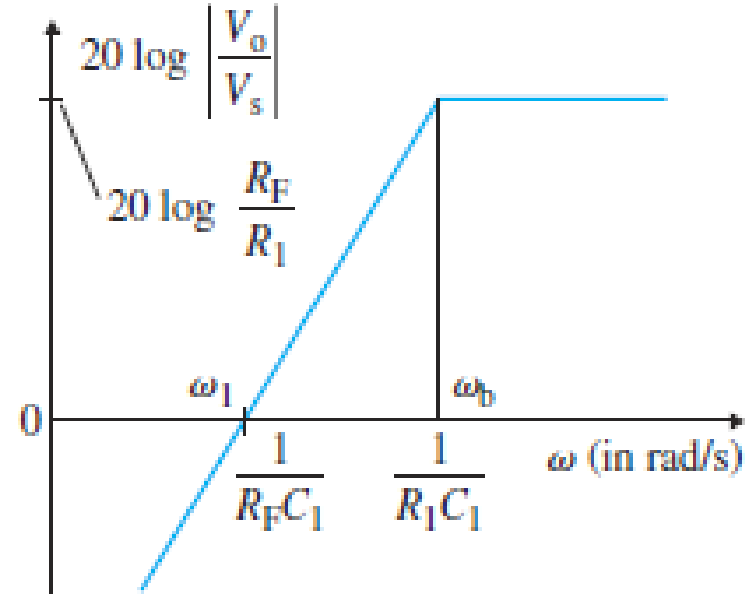


(b) Magnitude plot

# Addition-Subtraction Amplifiers


$$v_o = \left(1 + \frac{R_F}{R_B}\right) \left(\frac{R_A}{R_a} v_a + \frac{R_A}{R_b} v_b + \frac{R_A}{R_c} v_c\right) - \left(\frac{R_F}{R_1} v_1 + \frac{R_F}{R_2} v_2 + \frac{R_F}{R_3} v_3\right)$$

$$R_A = (R_a \parallel R_b \parallel R_c \parallel R_x)$$
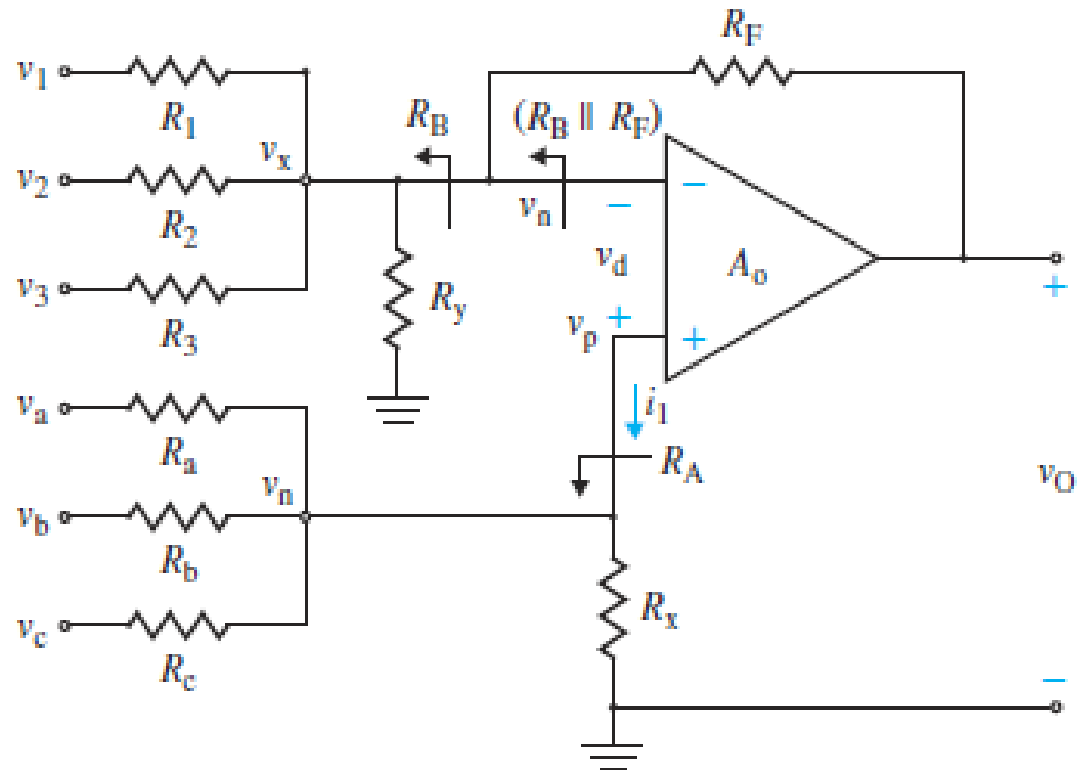
$$R_B = (R_1 \parallel R_2 \parallel R_3 \parallel R_y)$$



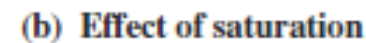
- The output voltage of the amplifier cannot exceed the positive saturation limit  $V_{O(max)}$  and cannot decrease below the negative saturation limit  $-V_{O(min)}$ .
- As long as the amplifier operates with the saturation limits, the voltage gain can normally be assumed to be linear.





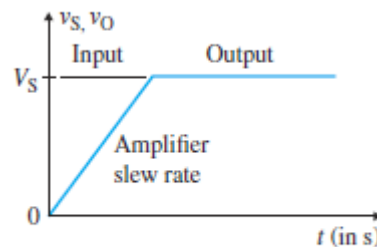
# Some Definitions on Op-Amps

- **Rise Time:** the time required for the output voltage to rise from 10% to 90% of the steady-state value.
- **Slew rate (SR):** the maximum rate of rise of the output voltage per unit time, and it is measured in volts per microsecond.




(a) Step input

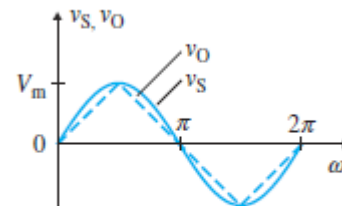

(b) Sinusoidal input

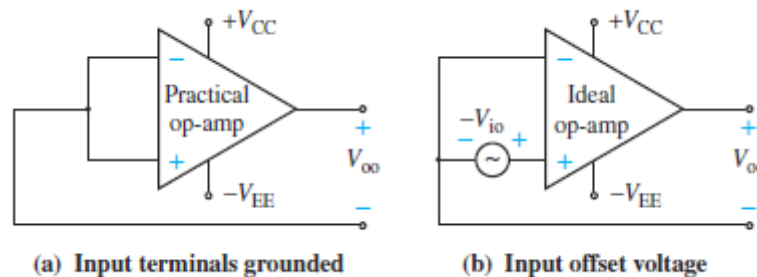
# Input Offset Voltage

- If the input terminals of an op-amp are tied together and connected to the ground, a certain DC voltage exits at the output. This voltage is called the output offset voltage  $V_{oo}$ .
- Any differential signal between the input terminals is amplified and gives the output voltage  $V_{oo}$ .



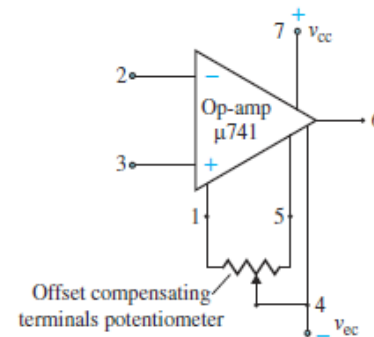
# Minimizing Output Offset Voltage

- Two ways to minimize the output offset voltage:
- (a) Compensating Network:



- (b) Capacitor Coupling:

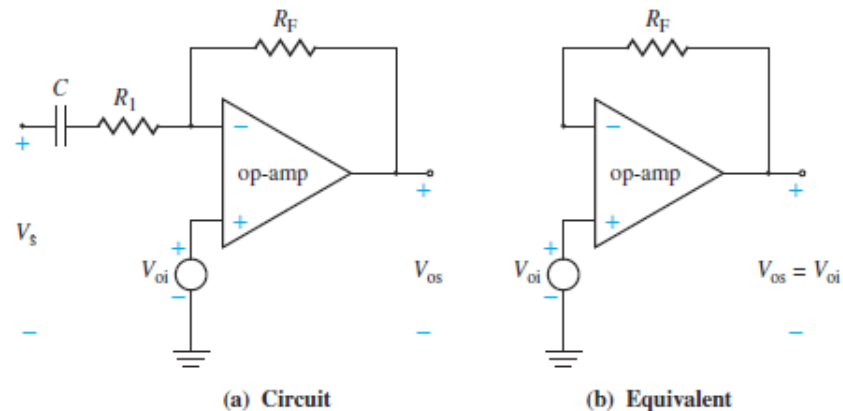


# Input Offset Current

- The DC input base currents will be equal only if the internal transistors have equal current gains (betas).
- The average value  $I_B$  is called the input bias current and is given by:

$$I_B = \frac{I_{B1} + I_{B2}}{2}$$


- Input offset current

$$I_{io} = |I_{B1} - I_{B2}|$$

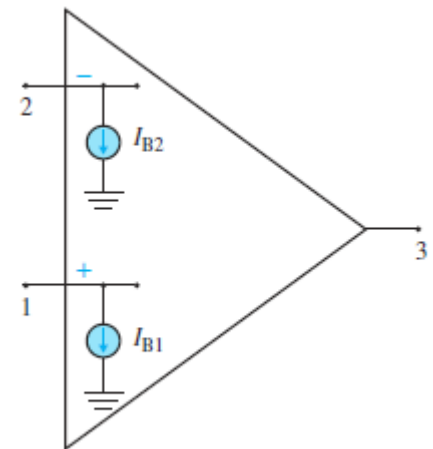

# Effect of Input Offset Current

$$V_+ = -R_x I_{B1}$$

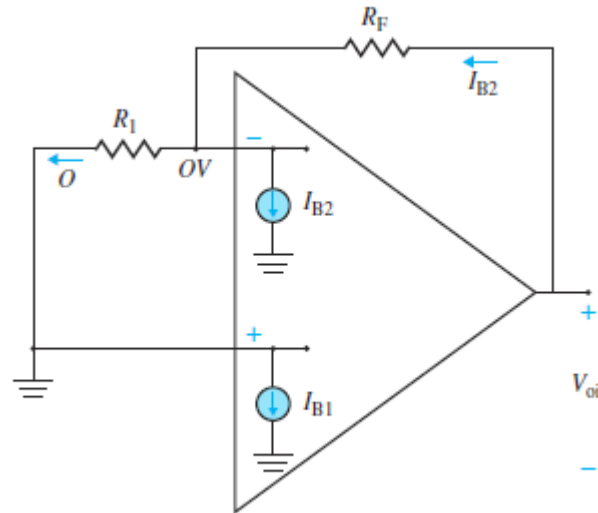

# Op-Amp Circuit Design

The design sequence:

- **Step 1.** Study the problem.
- **Step 2.** Create a block diagram of the solution.
- **Step 3.** Find a hand-analysis circuit-level solution.
- **Step 4.** Use PSpice/Multisim/SPICE for verification.
- **Step 5.** Construct the circuit in the lab and take measurements.

# Chapter 2 Summary

- An op-amp is a high-gain differential amplifier that can perform various functions in electronic circuits.
- The analysis of an op-amp circuit can be simplified by assuming ideal characteristics. An ideal op-amp has a very high voltage gain, a very high input resistance, a very low output resistance, and a negligible input current.
- The characteristics of practical op-amps differ from the ideal characteristics, but analyses based on the ideal conditions are valid for many applications and provide the starting point for practical circuit design.
- Although the DC model of op-amps can be used to analyze complex op-amp circuits, it does not take into account the frequency dependence and op-amp nonlinearities.